





Op amps taking the "raw" voltage off the sense resistors, and buffering it for the ADCs. Also protects the ADC inputs. Op amp output voltage is limited to VDDA, and they're cheap/easy to replace if damaged.

